



TRINITY COLLEGE FOR WOMEN NAMAKKAL

Department of Physics

DIGITAL ELECTRONICS

19UPHS04-ODD Semester

Presented by

Dr. R. SAKUNTHALADEVI

Assistant Professor

Department of Physics

<http://www.trinitycollegenkl.edu.in/>

OPERATIONAL AMPLIFIERS

INTRODUCTION



Typical IC packages




IC packages placed on circuit board

USES OF OP-AMP

- ❖ To provide voltage amplitude changes
- ❖ Comparators
- ❖ Oscillators
- ❖ Filter circuits
- ❖ Instrumentation circuits


OP-AMP BASICS

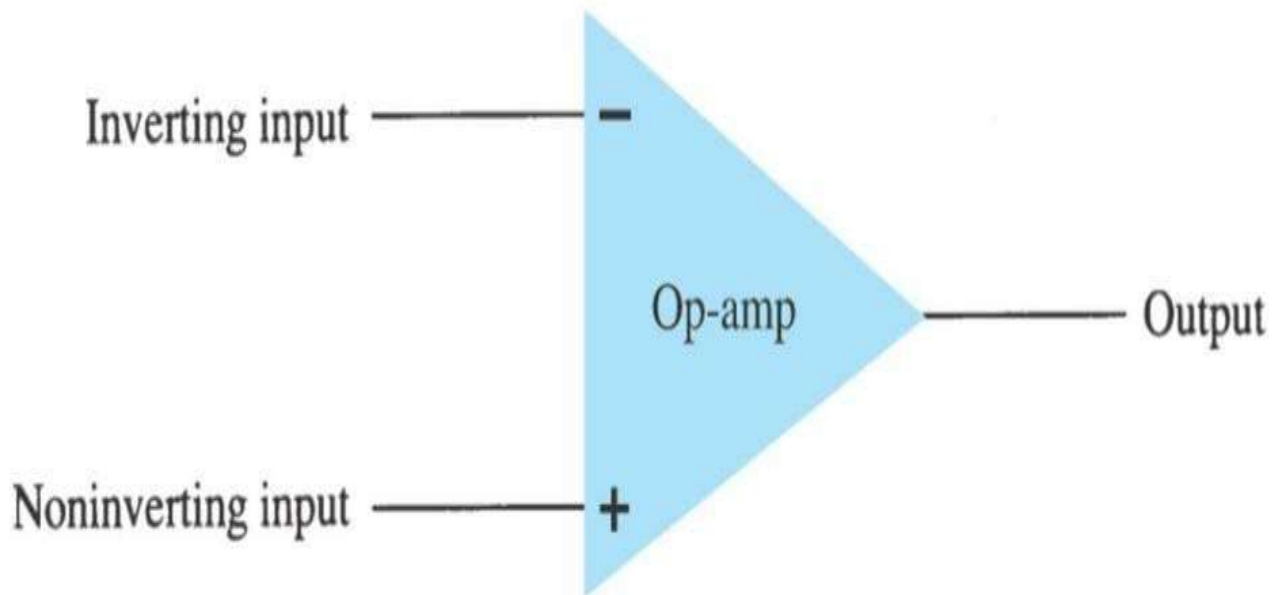

DEFINITION

- The operational amplifier is a circuit of components integrated into one chip.
- Op-amps were used to model the basic mathematical operations: addition, subtraction, integration, differentiation, and etc in electronic analog computers.
- A typical op-amp is powered by two dc voltages ($+V$ and $-V$) and has an inverting (-) and a non-inverting input(+) and an output.

IDEAL / PRACTICAL OP-AMP

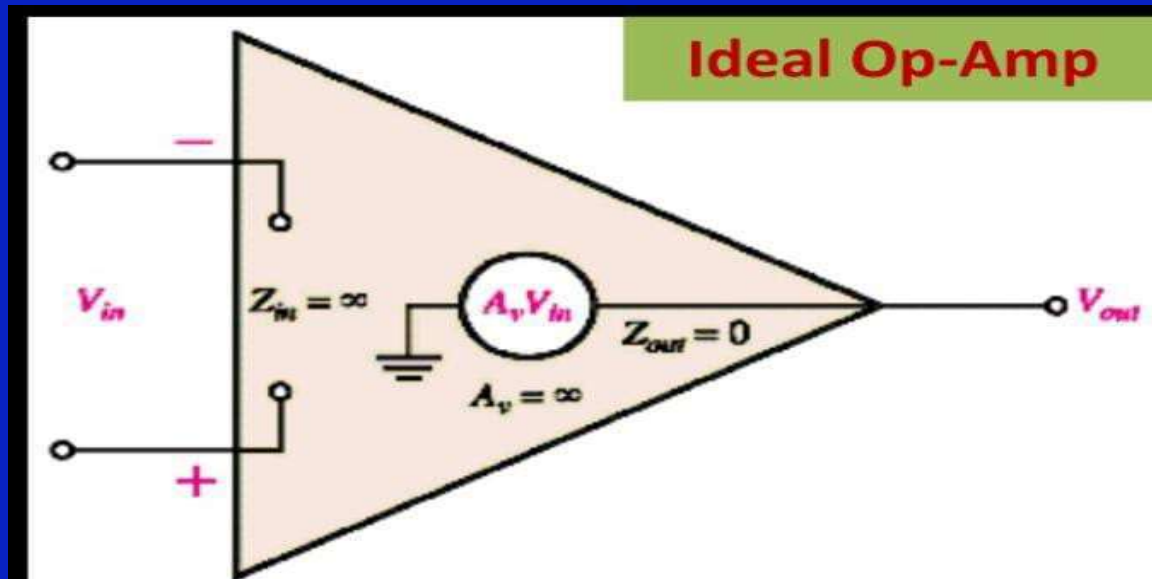

- Voltage gain (A_v) = Infinite
- Bandwidth = Infinite
- Input impedance (Z_{in}) = Infinite
- Output impedance (Z_{out}) = Zero

PROPERTIES

Ideal Op-Amp

- Infinite input impedance
- Zero output impedance
- Infinite open-loop gain
- Infinite bandwidth
- Zero noise contribution
- Both differential inputs stick together

Practical Op-Amp

Input impedance 500k-2M
Output impedance 20-100
Open loop gain (20k to 200k)
Noise contribution
Non-zero DC output offset

INPUT IMPEDANCE

- Input impedance (Z_{in}) is measured across the input terminals.
- It is the Thevenin resistance of the internal connection between the two input terminals.
- Input impedance (Z_{in}) is the ratio of input voltage (V_{in}) to input current (I_{in}).
- When $Z_{in} = \infty$, the input current (I_{in}) = 0.
- So any current will neither flow from the source supply into the amplifier's input circuitry, nor will it accept current from any external circuit.
- In real, the resistance is 500k to 2M.

OUTPUT IMPEDANCE

- The internal resistance of the op-amp is op-amp output impedance Z_{out} .
- This internal resistance is in series with the load reducing, the output voltage available to the load.
- The output impedance of the ideal operational amplifier is assumed to be zero acting as a perfect internal voltage source with no internal resistance, so that it can supply as much current as necessary to the load.
- Real op-amps have output impedance in the range 20-100

OPEN-LOOP GAIN (A_{01})

- Open-Loop gain, A_{01} is the gain of the op-amp without feedback.
- In the ideal op-amp, A_{01} is infinite.
- In the real op-amp is (20k to 200k).

THANK YOU

<http://www.trinitycollegenkl.edu.in/>